

METE 3100U
Actuators and Power Electronics

Lecture 20
Transient and Dynamics


Outline of Lecture 20

By the end of today's lecture, you should be able to

- Model a separately excited DC generator and motor
- Model the transient of DC generators
- Model the transient of DC motors to disturbances

Applications

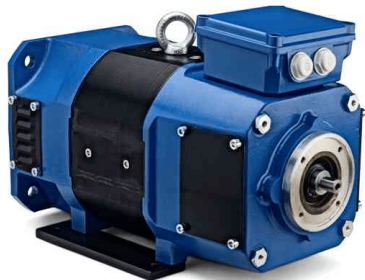How does a sudden change in the electrical load affect the resistance torque of the DC generator?



Applications

A sudden change in a synchronous motor load can make it lose synchrony.



DC generator transient

Assumptions:

→ No magnetic saturation

→ No mutual inductance

The back emf and torque due to the field rotation is


$$e_a = k_a \Phi \omega_m$$

$$T = k_a \phi i_a$$

If linearity is assumed

$$e_a = k_f i_f \omega_m$$

$$T = k_f i_f i_a$$

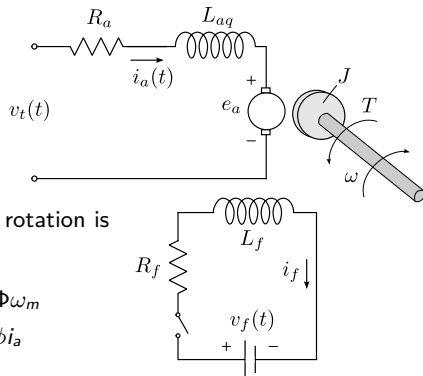

Field circuit transient

The machine rotates at a constant speed ω when the switch is closed


The field circuit equations is

$$V_f = R_f i_f + L_f \frac{di_f}{dt}$$
$$V_f(s) = I_f(s)(R_f + sL_f)$$

The transfer function is

$$\frac{I_f(s)}{V_f(s)} = \frac{1}{L_f s + R_f} = \frac{1}{R_f(1 + s\tau_f)} \quad (1)$$

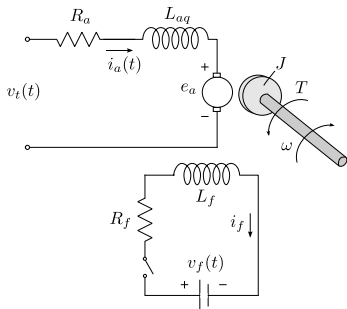where $\tau_f = L_f/R_f$ is the time constant.



Field circuit transient

The generated armature voltage is

$$e_a = k_f i_f \omega_m = k_g i_f$$

$$E_a(s) = k_g I_f(s)$$


The generated voltage to the field circuit voltage is

$$\frac{E_a(s)}{V_f(s)} = \frac{E_a(s)}{I_f(s)} = \frac{I_f(s)}{V_f(s)} = \frac{k_g}{R_f(1 + s\tau_f)}$$


In the time domain:

$$e_a(t) = \frac{k_g V_f}{R_f} (1 - e^{-\frac{t}{\tau_f}})$$
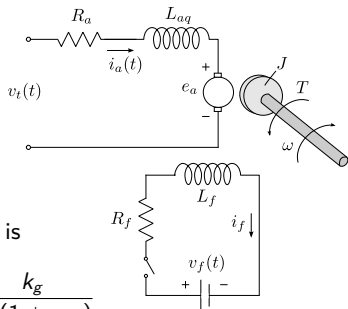
$$e_a(t) = E_a (1 - e^{-\frac{t}{\tau_f}})$$



Field circuit transient

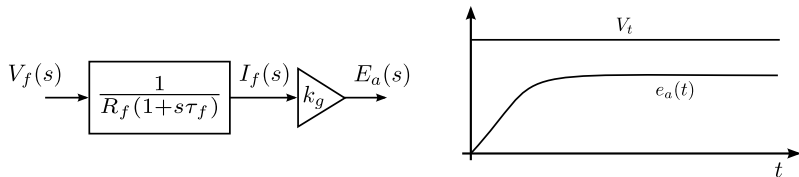

$$e_a(t) = \frac{k_g V_f}{R_f} (1 - e^{-\frac{t}{\tau_f}})$$

$$e_a(t) = E_a (1 - e^{-\frac{t}{\tau_f}})$$


where:

$\Rightarrow E_a = e_a(\infty) = \frac{k_g V_f}{R_f} = \frac{k_g}{I_g}$ is the steady-state generated voltage

$\Rightarrow I_f = \frac{V_f}{R_f}$ is the steady-state current

Armature circuit transient

Line load: R_L and L_L

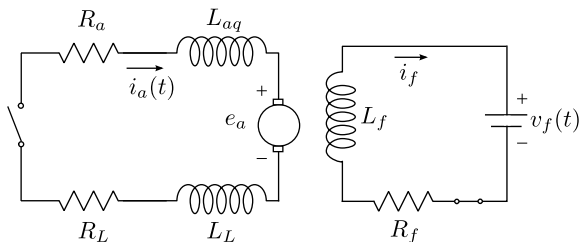

If the switch is closed when the rotation speed is constant

$$\begin{aligned} E_a &= R_a i_a + L_{aq} \frac{di_a}{dt} + R_L i_a + L_L \frac{di_a}{dt} \\ &= \underbrace{(R_a + R_L)}_{R_{at}} i_a + \underbrace{(L_{aq} + L_L)}_{L_{at}} \frac{di_a}{dt} \\ &= R_{at} i_a + L_{at} \frac{di_a}{dt} \end{aligned}$$

Armature circuit transient

The transfer function is

$$E = R_{at}I_a + L_{at}I(s)s \quad (2)$$

$$\frac{I_a(s)}{E_a(s)} = \frac{1}{R_{at}(1 + s\tau_{at})} \quad (3)$$

with $\tau_{at} = L_{at}/R_{at}$ is the armature circuit time constant.

The response to a step change of E_a is

$$i_a(t) = \frac{E_a}{R_{at}} \left(1 - e^{-\frac{t}{\tau_{at}}} \right) \quad (4)$$

The armature current to the **field voltage** is

$$\frac{I_a(s)}{V_f(s)} = \frac{I_a(s)}{E_a(s)} \frac{E_a(s)}{V_f(s)} = \frac{k_g}{R_f R_{at}(1 + sT_f)(1 + s\tau_{at})} \quad (5)$$

Field and armature transient

For a step input $V_f(s) = \frac{V_f}{s}$, the current is

$$I_a(s) = \frac{V_f k_g}{R_t R_{at} s (1 + s\tau_f)(1 + s\tau_{at})} \quad (6)$$

Partial fraction expansion yields:

$$I_a(s) = \frac{A_1}{s} + \frac{A_2}{s + 1/\tau_f} + \frac{A_3}{s + 1/\tau_{at}} \quad (7)$$




where

$$A_1 = \left. \frac{A}{(s + 1/\tau_f)(s + 1/\tau_{at})} \right|_{s=0} = A\tau_f\tau_{at} \quad A = k_g V_f / R_f R_{at} \tau_f \tau_{at}$$
$$A_2 = \left. \frac{A}{s(s + 1/\tau_{at})} \right|_{s=-1/\tau_f} \quad A_3 = \left. \frac{A}{s(s + 1/\tau_f)} \right|_{s=-1/\tau_{at}}$$

The time domain response is

$$i_a(t) = A_1 + A_2 e^{-\frac{t}{\tau_f}} + A_3 e^{-\frac{t}{\tau_{at}}} \quad (8)$$

Field and armature transient

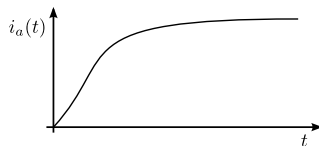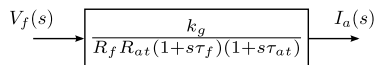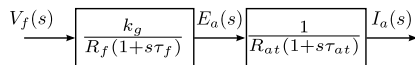

A_1 is the steady-state armature current

$$A_1 = i_a \infty = (k_g V_f) / (R_f R_{at}) = k_g I_f / R_{at} = E_a / R_{at}$$

Separately-excited DC motor transient

Assuming magnetic linearity:

$$T(s) = k_f I_a(s)(i_f) = k_m I_a(s)$$

$$E_a(s) = k_f \omega(s)(i_f) = k_m \omega(s)$$


where $k_m = i_f k_f$ is a constant.

$$V_t(s) = E_a(s) + R_a I_a(s) + L_{aq} s I_a(s)$$

$$V_t(s) = k_m \omega(s) + R_a I_a(s) + L_{aq} s I_a(s)$$

$$V_t(s) = k_m \omega(s) + I_a(s) R_a (1 + s \tau_a)$$

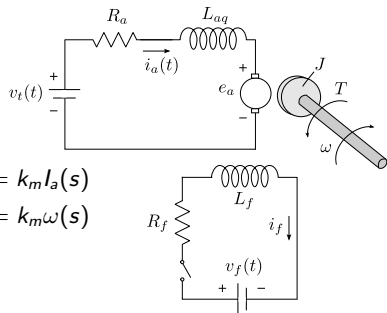with $\tau_a = L_{aq}/R_a$ is the armature electrical time constant.



Separately-excited DC motor transient



For the mechanical system

$$T(s) = k_m I_a(s) = J s \omega(s) + b \omega(s) + T_L(s)$$

For the electromechanical system

$$\omega(s) = \frac{T(s) - T_L(s)}{b(1 + sJ/b)} = \frac{k_m I_a(s) - T_L(s)}{b(1 + s\tau_m)}$$
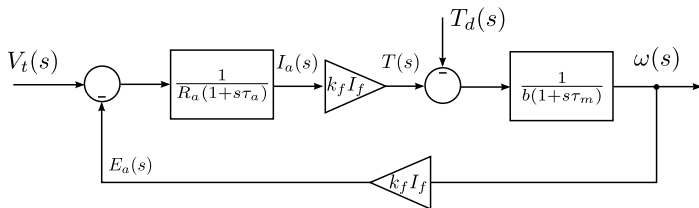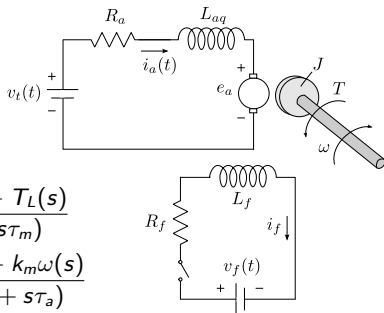
$$I_a(s) = \frac{V_t(s) - E_a(s)}{R_a(1 + L_{aq}/R_a)} = \frac{V_t(s) - k_m \omega(s)}{R_a(1 + s\tau_a)}$$



Separately-excited DC motor transient

Scenario 1: Load torque proportional to speed


$$T_L(s) = b_L \omega \quad (9)$$

thus

$$T(s) = Js\omega(s) + (b + b_L)\omega(s) \quad (10)$$

The load increases the viscous friction. The transfer function is
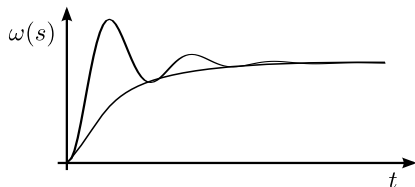
$$\frac{\omega(s)}{V_t(s)} = \frac{k_m}{k_m^2 + bR_a(1 + s\tau_m)(1 + s\tau_a)} \quad (11)$$



Separately-excited DC motor transient

Scenario 2: Armature inductance is negligible $\tau_a = 0$

$$\frac{\omega(s)}{V_t(s)} = \frac{k_m}{k_m^2 + bR_a(1 + s\tau_m)} \quad (12)$$

What is the time response?

Scenario 3: No friction, $b = 0$, with an inertial load J_L

$$T(s) = k_m I_a(s) = (J + J_s)s\omega(s) \quad (13)$$

thus

$$\frac{\omega(s)}{V_t(s)} = \frac{k_m}{k_m^2 + R_a(J + J_L)s(1 + s\tau_a)} \quad (14)$$

Separately-excited DC motor transient

Scenario 4: Supply disconnected ($v_t(t) = 0$ at $t = t_1 > 0$ with $\omega(t_1) \neq 0$)


$$T(t) = k_m i_a(t) = J s \omega(t) + b \omega(t) = 0 \quad (15)$$

or $b \omega(t) = -J \frac{d\omega}{dt}$. For an initial speed $\omega(t = t_1) = \omega_0$:

$$b \omega(s) = -J[s\omega(s) - \omega_0] \rightarrow \omega(s) = \frac{\omega_0}{(s + b/J)} = \frac{\omega_0}{s + 1/\tau_m} \quad (16)$$


The time domain response is
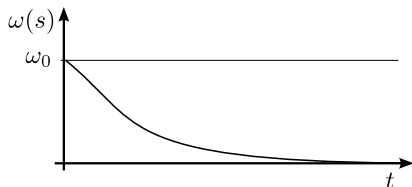
$$\omega(t) = \omega_0 e^{-\frac{t}{\tau_m}} \quad (17)$$




Synchronous machines

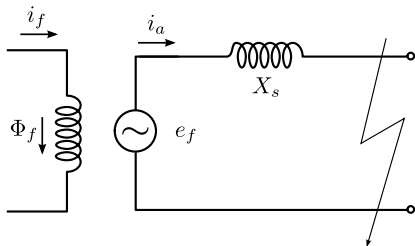The rotor rotates at a constant speed and induces a voltage e_f in the stator




Motor terminals are shorted:

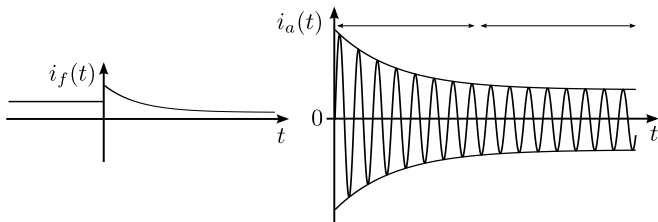


Induction machines

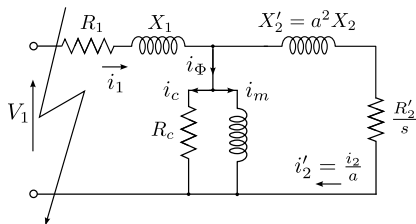The rotor rotates at a constant speed with a constant current i_1



Motor terminals are shorted:

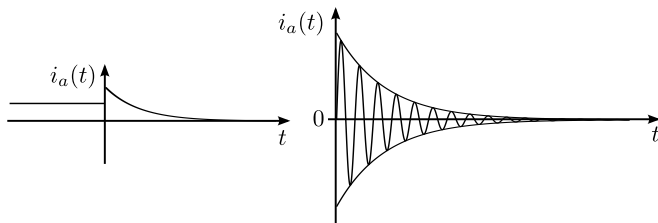


Exercise 92


A separately-excited DC generator is driven at rated speed when a field circuit voltage is suddenly applied to the field winding.

Determine:


- (a) The armature-generated voltage as a function of time
- (b) The steady-state armature voltage
- (c) The time required to rise the armature voltage to 90% of the steady-state value

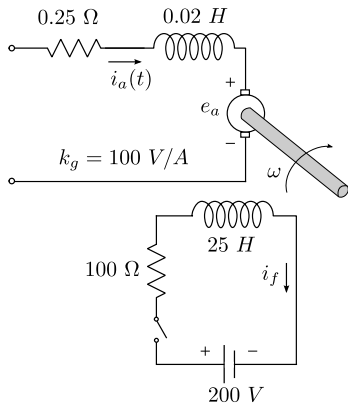

Exercise 92 - continued

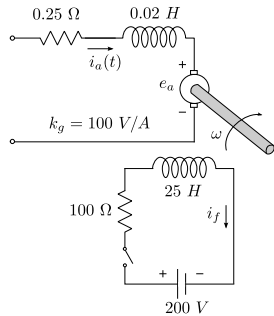


Exercise 92 - continued

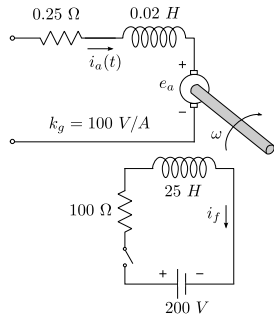

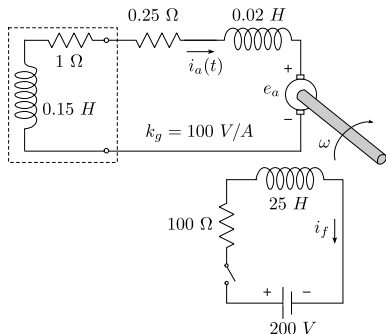
Exercise 93

A separately-excited DC generator is driven at rated speed and a load is connected in series to the generator terminals.





If a field voltage of $200 V$ is suddenly applied to the field winding, determine the armature current as a function of time.

Exercise 93 - continued

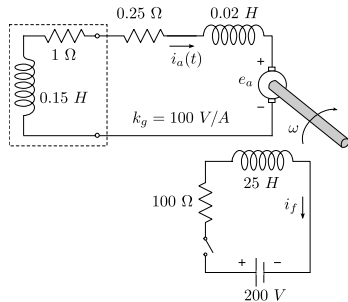


Exercise 93 - continued

$$i_a(t) = 160 - 351e^{-4t} + 191e^{-7.35t}$$

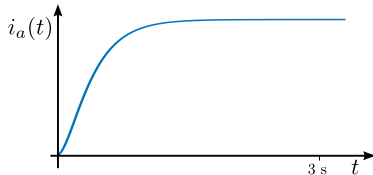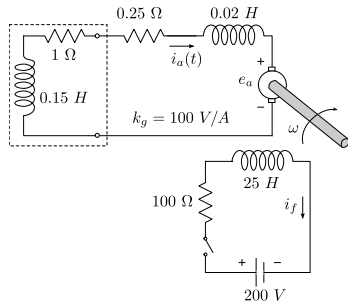

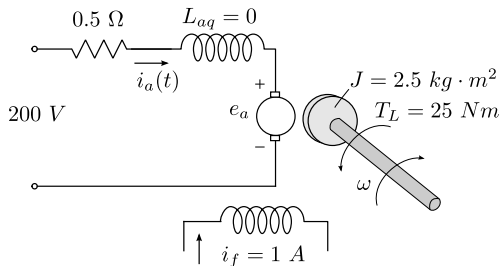Exercise 94

The separately excited DC motor generates an open-circuit armature voltage of 220 V when it runs at 2000 rpm with a field current of 1 A.




The motor drives a constant load of $T_L = 25 \text{ N} \cdot \text{m}$. The combined inertia of motor and load is $J = 2.5 \text{ kg} \cdot \text{m}^2$. The armature terminals are connected to a 220 V DC source and the field current is 1 A.


Determine the expressions for the speed and armature current as a function of time, and the steady-state values.

Exercise 94 - continued


$v_t = 200$ V, no load, 2000 rpm, $i_f = 1$ A.

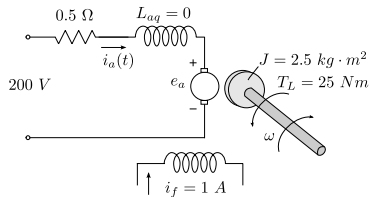


Exercise 94 - continued

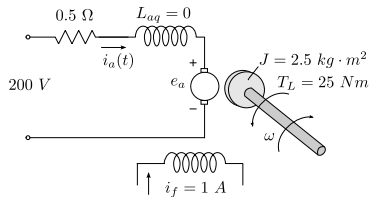

Exercise 94 - continued

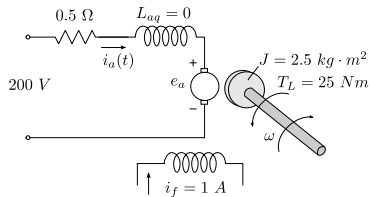


Exercise 94 - continued

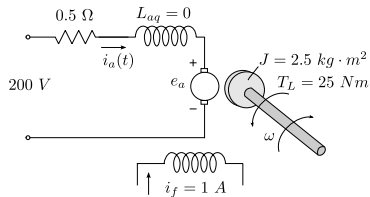

Exercise 95

A separately excited DC generator is driven at 1200 rpm with a field current of 2 A. The armature is then suddenly connected to the load.

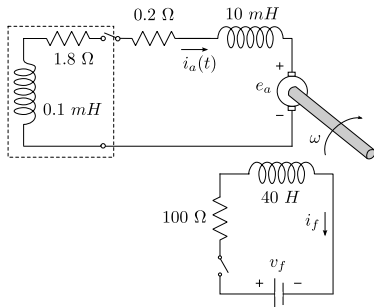- (a) Determine the load terminal voltage as a function of time.
- (b) Determine the steady-state terminal voltage
- (c) Determine the torque as a function of time




At 1000 rpm, the field constant is $k_g = 100$ V per field ampère.

Exercise 95 - continued

(a) Determine the load terminal voltage as a function of time.


→ 1000 rpm - $k_g = 100$ V/A.

→ 1200 rpm - $k_g = ?$

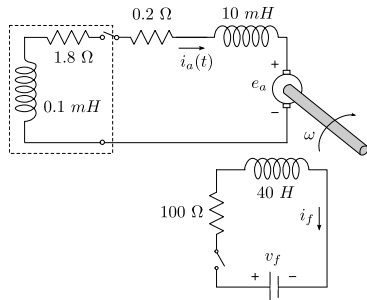


Exercise 95 - continued

(a) The load terminal voltage as a function of time.

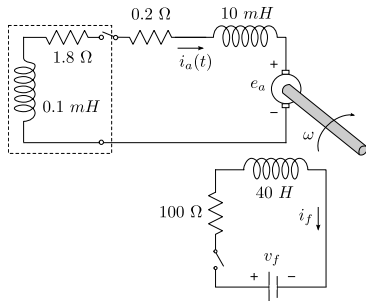

Exercise 95 - continued

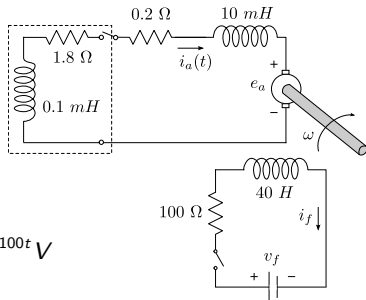
(b) The load terminal steady-state voltage.



$$v_t(t) = 216 - 96e^{-100t} \text{ V}$$

Exercise 95 - continued

(c) The torque as a function of time

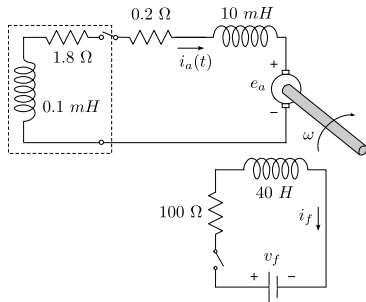


Exercise 96

The separately excited DC motor drives a load whose torque is proportional to the speed. The field current is held constant at the rated value when a voltage is suddenly applied across the armature terminals.

Determine:

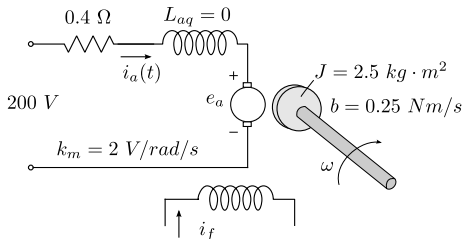
- The motor speed as a function of time.
- The steady-state speed ω_{ss} .
- The time required to reach 95% of ω_{ss} .
- The current $i_a(t)$.



b and J include the motor and load characteristics.

Exercise 96 - continued

(a) The motor speed as a function of time.

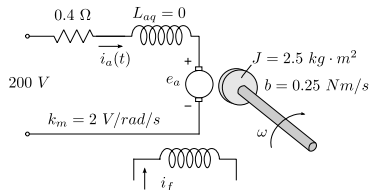


Exercise 96 - continued

(b) The steady-state speed ω_{ss} .


$$\omega(t) = 97.6(1 - e^{-4.1t})$$

(c) The time required to reach 95% of ω_{ss} .

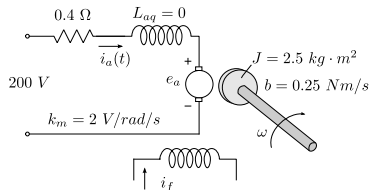

Exercise 96 - continued

(d) The current $i_a(t)$.

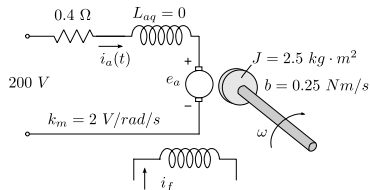


Exercise 97

The separately excited DC motor operates at no-load with $v_t = 200$ V and $i_f = 2$ A. Rotational losses are negligible. The motor is intended to be stopped by plugging, that is, by reversal of its armature voltage ($v_t' = -220$ V).


Determine:

- The no-load speed.
- The expression for the speed after plugging.
- The time required to stop.

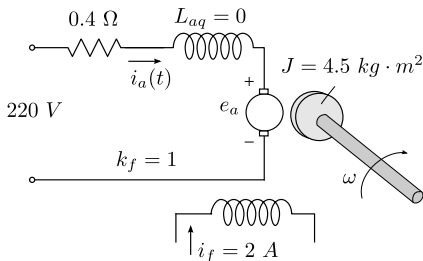


Exercise 97 - continued

(a) The no-load speed.

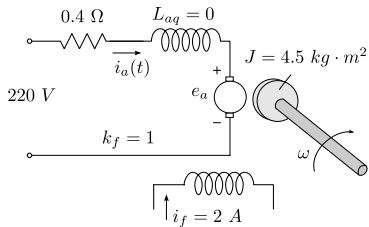


Exercise 97 - continued

(b) The expression for the speed after plugging.

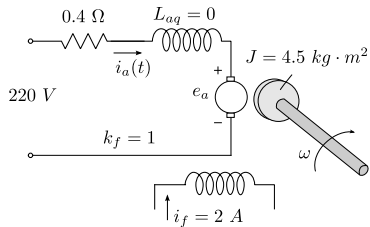

Exercise 97 - continued

(c) The time required to stop.

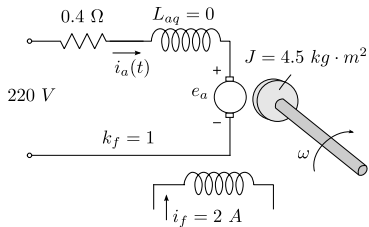

Next class...

- Final course review