

METE 3100U  
Actuators and Power Electronics

Lecture 4  
Diode Rectifiers


## Outline of Lecture 4

In today's lecture we will

- Review the principles of diodes
- Analyse and design diode rectifier circuits
- Determine the effects of load inductance on the load current

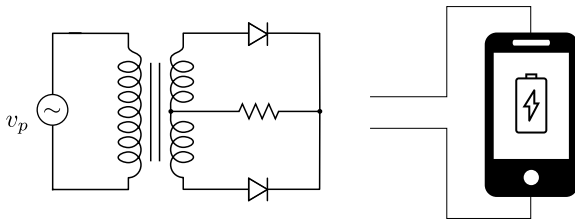
## Applications

A rectifier converts alternating current to direct current. The process is known as rectification, since it "straightens" the direction of current.





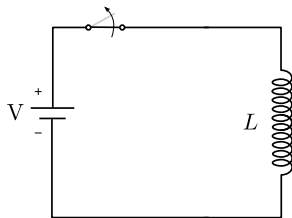
## Applications

For highly inductive load, how can the energy stored in the inductor be dissipated when the circuit is turned off?



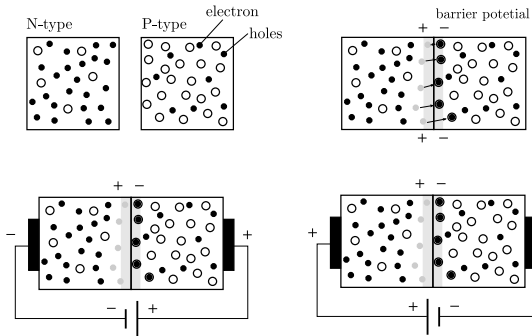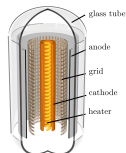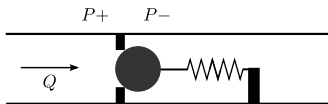
# Diode working principle

A diode is a semiconductor with two terminals allowing the flow of current in one direction only.





## Ideal vs practical diodes

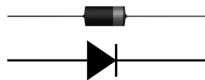




Operation modes:

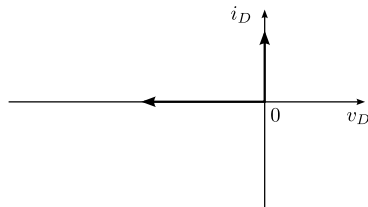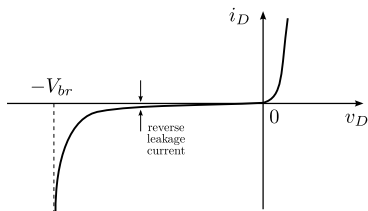- Forward-biased region:  $v_D > 0$ , the diode conducts
- Reverse-biased region:  $v_D < 0$ , the diode does not conduct
- Breakdown region:  $v_D < -V_{br}$ , the current is reversed


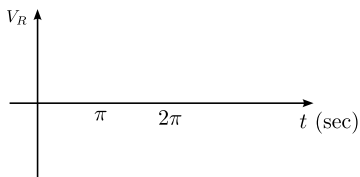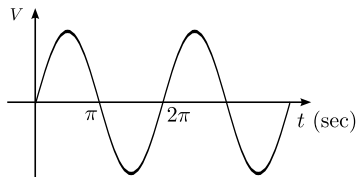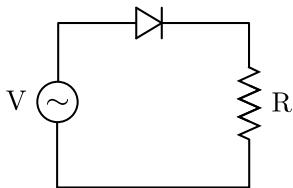
## Diode rectification


Diodes can be used to convert an alternating voltage (AC) into a continuous voltage (DC)



The average output voltage is

$$V_R = \frac{1}{T} \int_0^T V(t) dt \quad (1)$$

## Diode-switched LC load

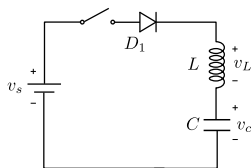

$$v_s = L \frac{di}{dt} + \frac{1}{C} \int_{t_0}^t i dt + v_c(t=0) \quad (2)$$

With no initial conditions ( $i(0) = 0$ ,  $v_c(0) = 0$ ) the Laplace transform gives:

$$V_s(s) = LI(s)s + \frac{I(s)}{Cs} \rightarrow I(s) = \frac{V_s}{L(s^2 + \omega_n^2)} \quad (3)$$

where  $\omega_n = 1/\sqrt{LC}$  and  $i(t) = \mathcal{L}^{-1}I(s)$ , thus:


$$i(t) = v_s \sqrt{\frac{C}{L}} \sin(\omega_n t) \quad (4)$$


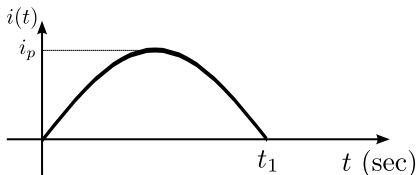
## Diode-switched LC load


The current is:

$$i(t) = v_s \sqrt{\frac{C}{L}} \sin(\omega_n t) \quad (5)$$




And the voltage  $v_c$  across the capacitor is:
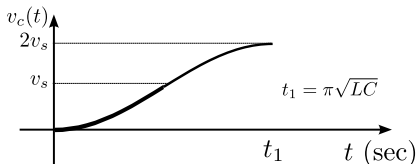
$$v_c(t) = \frac{1}{C} \int_0^t i dt = v_s (1 - \cos(\omega_n t)) \quad (6)$$



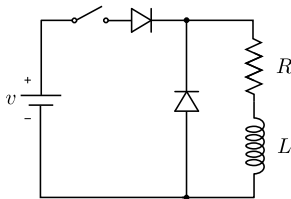
## Freewheeling diodes


→ Eliminates the sudden voltage spike across inductive loads when its supply current is suddenly reduced.



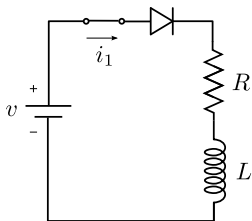Circuit **mode 1** - The switch is closed. The current is:



## Freewheeling diodes


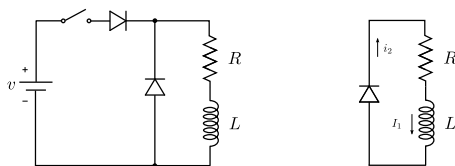


Circuit **mode 2** - The switch is opened and  $i_L = I_1$ . The current is:

$$0 = L \frac{di_2}{dt} + Ri_2 \quad (7)$$


With the initial condition  $i_2(0) = I_1$ , the current becomes
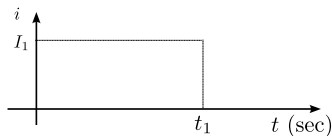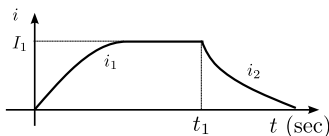
$$i_2(t) = I_1 e^{-\frac{R}{L}t} \quad (8)$$



## Recovery of trapped energy

The trapped energy in the transformer can be returned to the primary source.

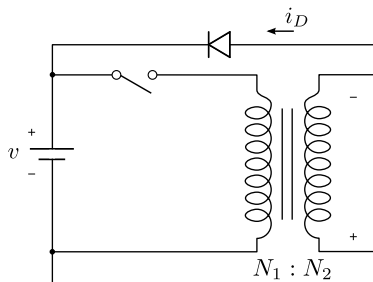


**Mode 1** - The switch is closed:  $i_D = 0$ .


**Mode 2** - The switch is open: The voltage across the inductor is reversed:  
 $i_D \neq 0$
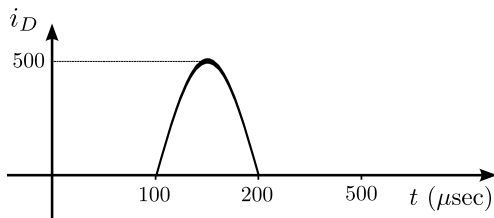
## Exercise 10

The current waveform of a diode is shown in the figure. Determine the average, and the peak current of the diode. Assume a half sine wave.




## Exercise 10 - continued

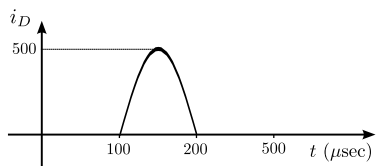

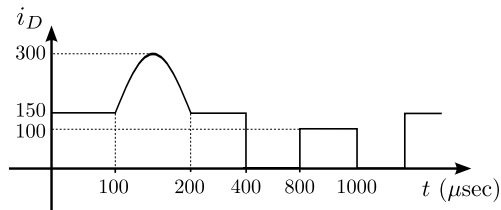
## Exercise 11

The waveforms of the current flowing through a diode is shown in the figure. Determine the average, rms, and peak current ratings of the diode. Assume a half sine wave of 150 A (peak)





## Exercise 11 - continued

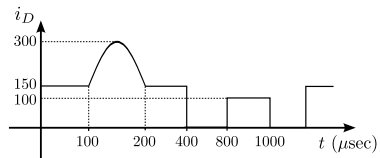


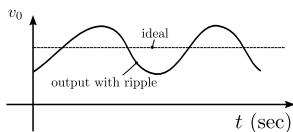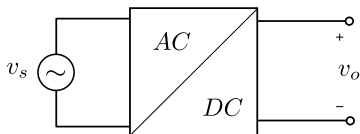
## Diode rectifiers

Rectifiers convert AC current to DC current



→ A rectifier is a power processor

→ Input voltage and current must remain in phase

Output AC power:

$$P_{ac} = V_{rms} I_{rms} \quad (9)$$

Output DC power:



$$P_{dc} = V_{dc} I_{dc} \quad (10)$$

Rectification ratio:

$$\eta = \frac{P_{dc}}{P_{ac}} \quad (11)$$
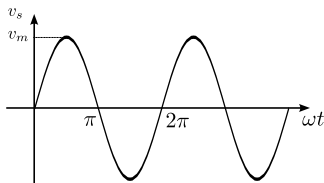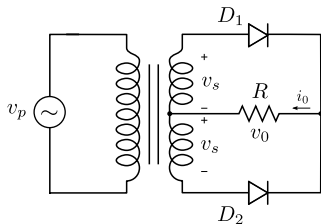
## Single phase full wave rectifiers


Centre-tapper transformer rectifier: An additional wire is connected across the middle of the secondary winding of a transformer



The average load voltage is



$$V_0 = \frac{2}{T} \int_0^{\frac{T}{2}} v_s \sin(\omega t) d\omega t$$

$$V_0 =$$

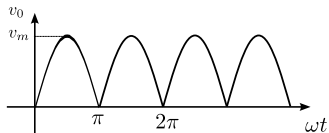
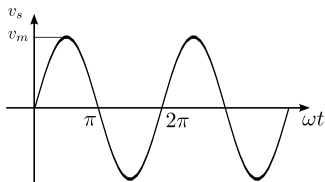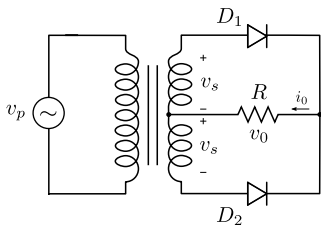
## Single phase full wave rectifiers


Centre-tapper transformer rectifier: An additional wire is connected across the middle of the secondary winding of a transformer




The root mean square (rms) voltage is

$$V_0 = \sqrt{\frac{2}{T} \int_0^{\frac{T}{2}} [v_s \sin(\omega t)]^2 d\omega t}$$
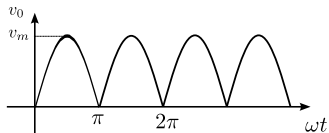
$$V_0 = \frac{V_m}{\sqrt{2}} = 0.707 v_s$$



## Bridge rectifier with RL load

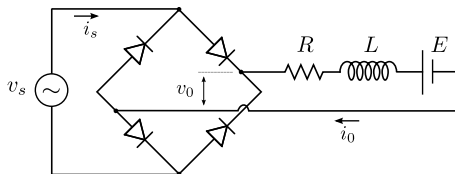


The generator voltage is


$$v_s = (V_s\sqrt{2}) \sin \omega t \quad (12)$$

where  $V_s$  is the RMS input voltage. The voltage  $v_o$  across the load

$$v_o = \underbrace{|(V_s\sqrt{2}) \sin \omega t|}_{v_m} \quad (13)$$

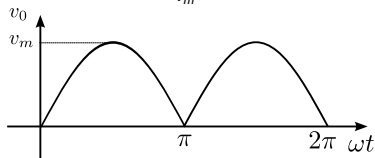

## Bridge rectifier with RL load

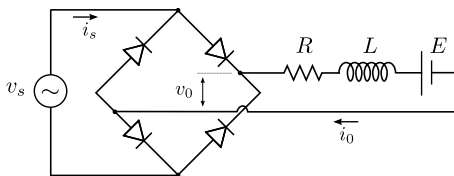

The load current is


$$L \frac{di_0}{dt} + Ri_0 + E = |\sqrt{2}V_s \sin \omega t| \quad \forall i_0 > 0 \quad (14)$$

which has a solution of the form

$$i_0 = \left| \frac{\sqrt{2}V_s}{Z} \sin(\omega t - \theta) + ke^{-\frac{R}{L}t} - \frac{E}{R} \right| \quad (15)$$

with  $Z = \sqrt{R^2 + (\omega L)^2}$  and  $\theta = \tan^{-1}(\omega L/R)$ .

## Bridge rectifier with RL load

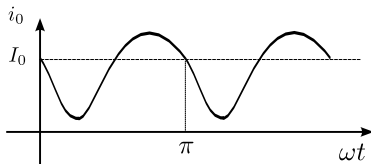

$I_0$  is the steady state current. At  $\omega t = \pi$ , we set  $i_0 = I_0$ , thus

$$k = \left( I_0 + \frac{E}{R} - \frac{\sqrt{2}V_s}{Z} \sin \theta \right) e^{\frac{R}{L} \frac{\pi}{\omega}} \quad (16)$$


Replacing the above in (15) yields:

$$i_0 = \frac{\sqrt{2}V_s}{Z} \sin(\omega t - \theta) + \left( I_0 + \frac{E}{R} - \frac{\sqrt{2}V_s}{Z} \sin \theta \right) e^{\frac{R}{L}(\frac{\pi}{\omega} - t)} - \frac{E}{R} \quad (17)$$

Steady-state:  $I_0 = i_0(\omega t = 0) = i_0(\omega t = \pi)$

$$I_0 = \frac{\sqrt{2}V_s}{Z} \sin(\theta) \frac{1 + e^{-(R/L)(\pi/\omega)}}{1 - e^{-(R/L)(\pi/\omega)}} - \frac{E}{R} \quad (18)$$

## Bridge rectifier with RL load

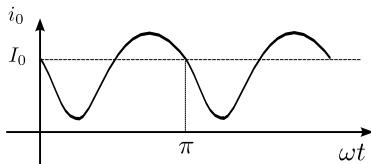

Finally, the current across the load is





$$i_0 = \frac{\sqrt{2}V_s}{Z} \left[ \sin(\omega t - \theta) + \frac{2}{1 - e^{-(R/L)(\pi/\omega)}} \sin \theta \left( e^{-\frac{R}{L}t} \right) \right] - \frac{E}{R} \quad (19)$$

with  $Z = \sqrt{R^2 + (\omega L)^2}$  and  $\theta = \tan^{-1}(\omega L/R)$ .

The average current  $i_{av}$  and rms current  $i_{rms}$  are

$$i_{av} = \frac{1}{2\pi} \int_0^\pi i_0 d(\omega t) \quad i_{rms} = \sqrt{\frac{1}{2\pi} \int_0^\pi i_0^2 d(\omega t)} \quad (20)$$



## Bridge rectifier with RL load

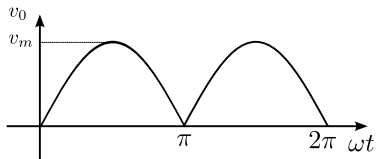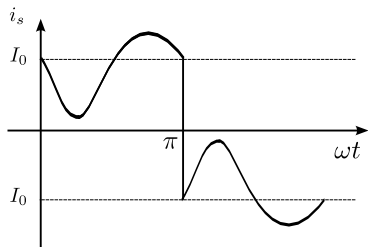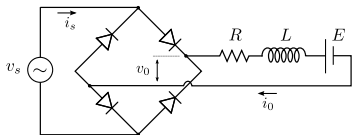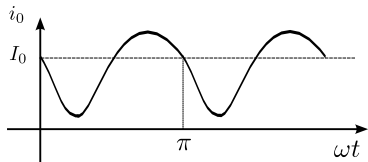




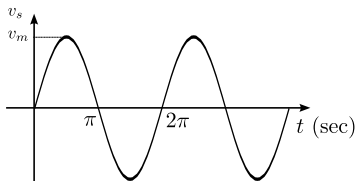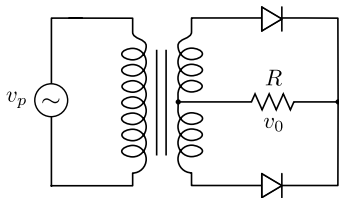
## Exercise 12

The single phase bridge rectifier has a purely resistive load  $R = 5\Omega$ , a peak supply voltage  $V_m = 170\text{ V}$ , and a supply frequency of 60 Hz. Determine the average output voltage of the rectifier if the source inductance is negligible.





## Exercise 12 - continued

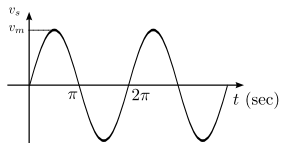
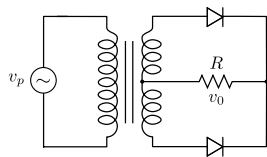

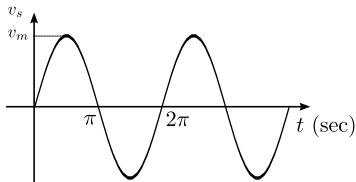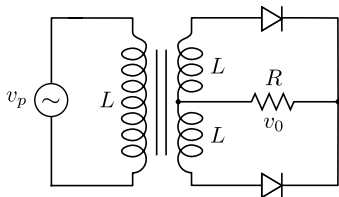
## Exercise 13

The single phase bridge rectifier has a purely resistive load  $R = 5\Omega$ , a source inductance per phase including the transformer leakage inductance of  $0.5\text{ mH}$ , a peak supply voltage  $V_m = 170\text{ V}$ , and a supply frequency of  $60\text{ Hz}$ . Determine the average output voltage of the inductor.





## Exercise 13 - continued

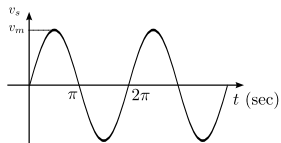
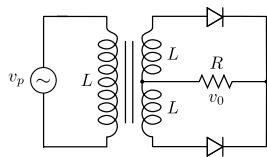

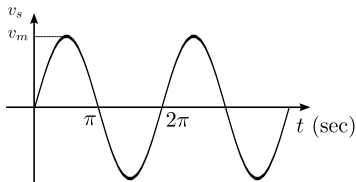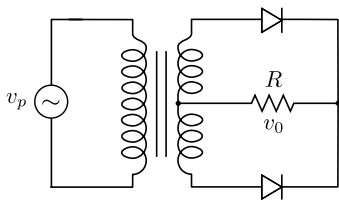
## Exercise 14



The bridge rectifier shown is required to supply an average voltage of  $V_{dc} = 240 \text{ V}$  to a resistive load of  $R = 10\Omega$ . Determine the required kVA rating of the transformer. Neglect all inductances.



## Exercise 14 - continued

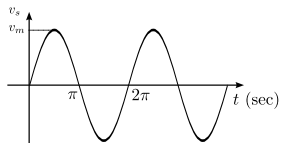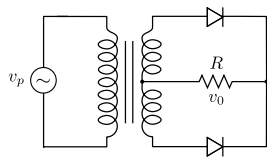

## Exercise 14 - continued

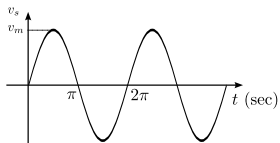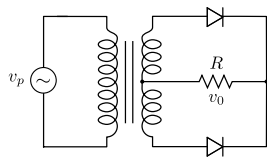

## Next class...

- DC/DC converters

Additional supporting materials for Lecture 4:

Diode working principle: <https://goo.gl/mncLJR>

RMS and average voltages: <https://goo.gl/xaiN2C>